



CHITTAGONG UNIVERSITY OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRONICS AND TELECOMMUNICATION ENGINEERING

VLSI Technology Sessional

ETE 404

Project

BCD to Excess-3 Decoder

Name: Anik Paul

ID: 1908054

Level: 04, Term: 01

Date of Submission: 10-11-2024

Full schematic view in cadence:

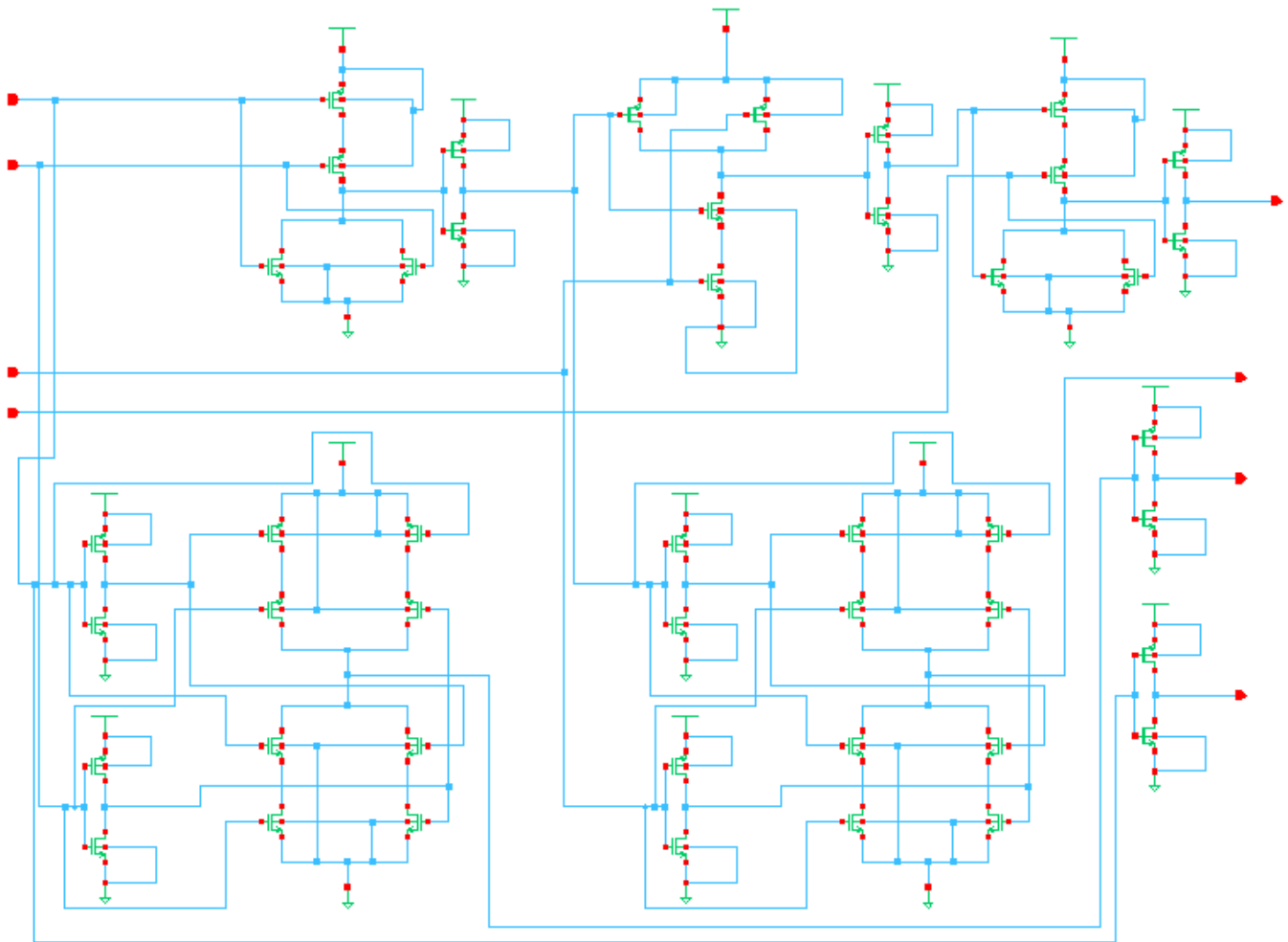


Fig. 1: Full schematic of BCD to Excess-3 Decoder

The Gates that are used:

NOT:

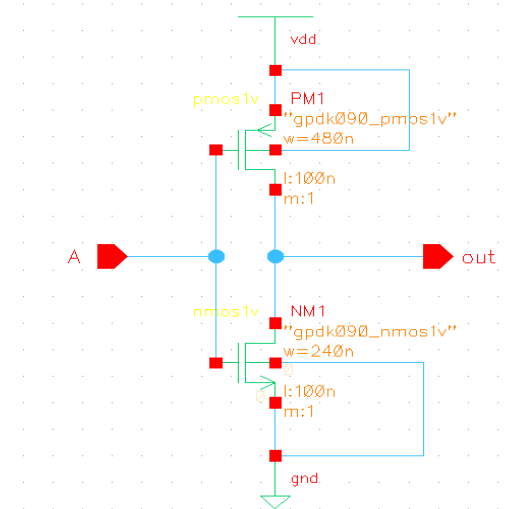


Fig. 2: Schematic of NOT gate

AND:

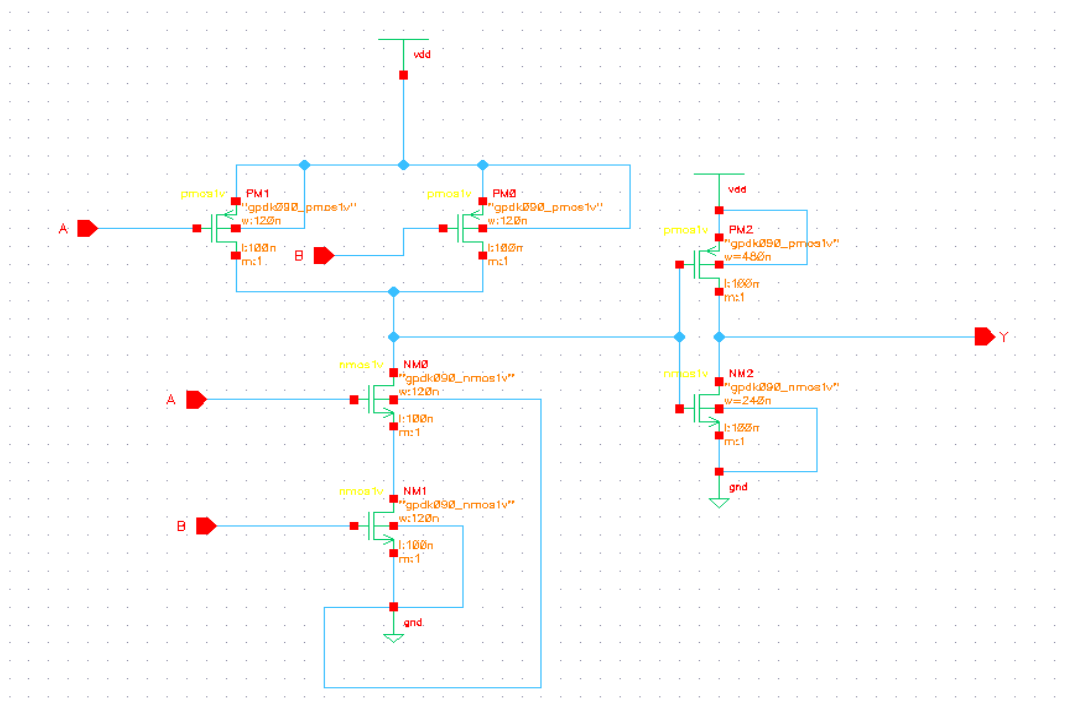


Fig. 3: Schematic of AND gate

OR:

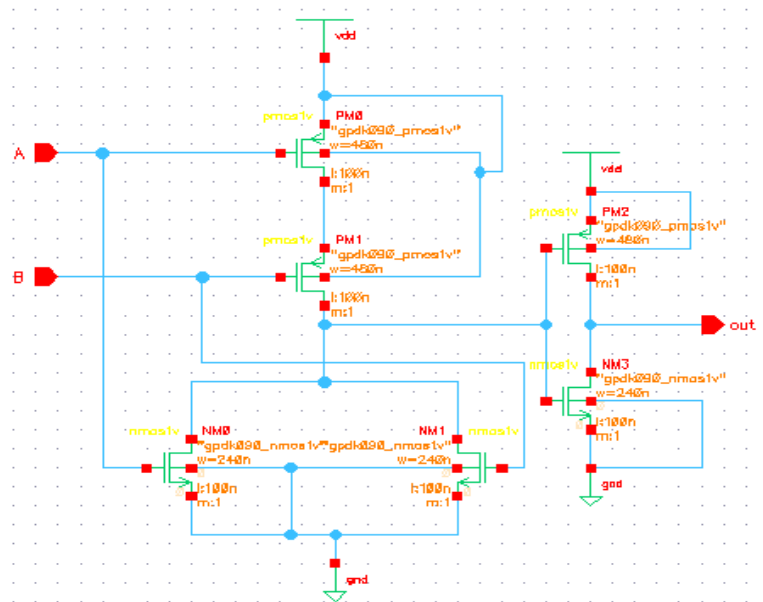


Fig. 4: Schematic of AND gate

X-OR:

 


Fig. 5: Schematic of X-OR gate

OUTPUT:

 


Fig. 6: Output of BCD to Excess-3 Decoder

Power graph:

 


Fig. 7: Power graph of BCD to Excess-3 Decoder

Power measurement:

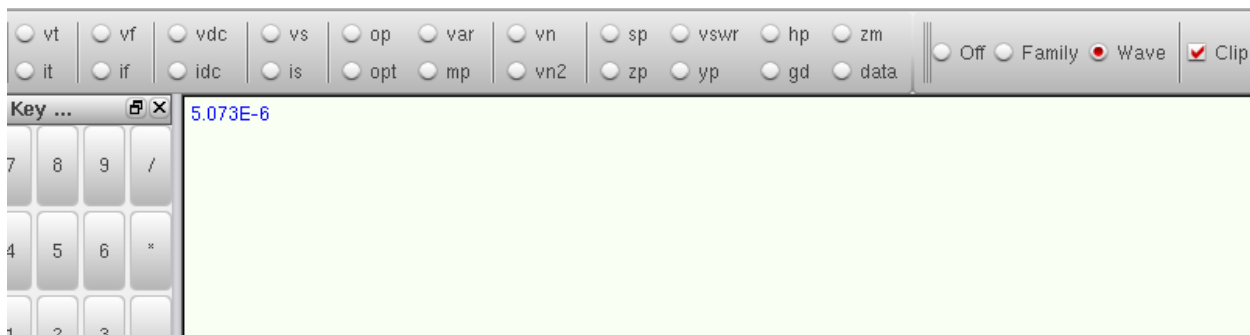


Fig. 8: Power measurement of BCD to Excess-3 Decoder